

## PHYS 331: Junior Physics Laboratory I

### Notes on Digital Circuits

Digital circuits are collections of devices that perform logical operations on two logical states, represented by voltage levels. Standard operations such as AND, OR, INVERT, EQUIVALENT, etc. are performed by devices known as gates. Groups of compatible gates can be combined to make yes/no decisions based on the states of the inputs. For example, a simple warning light circuit might check several switch settings and produce a single yes/no output. More complicated circuits can be used to manipulate information in the form of decimal digits, alphanumeric characters, or groups of yes/no inputs. These notes are intended to familiarize you with the elementary principles of this field.

#### A. Analysis of asynchronous logic

Suppose we have a statement which can be true or false, perhaps representing the presence or absence of a particle, a light signal on or off, a voltage present or absent, or any other binary possibility. For now we will ignore the physical meaning of the statement and ask how one would decide the logical truth or falsehood of combinations of such statements, a subject called combinatoric logic. If we denote the "truth value" of a statement  $A$  by 0 or 1, the standard combinations are shown in the form of "truth tables" in Fig. 1. These basic combinations, or

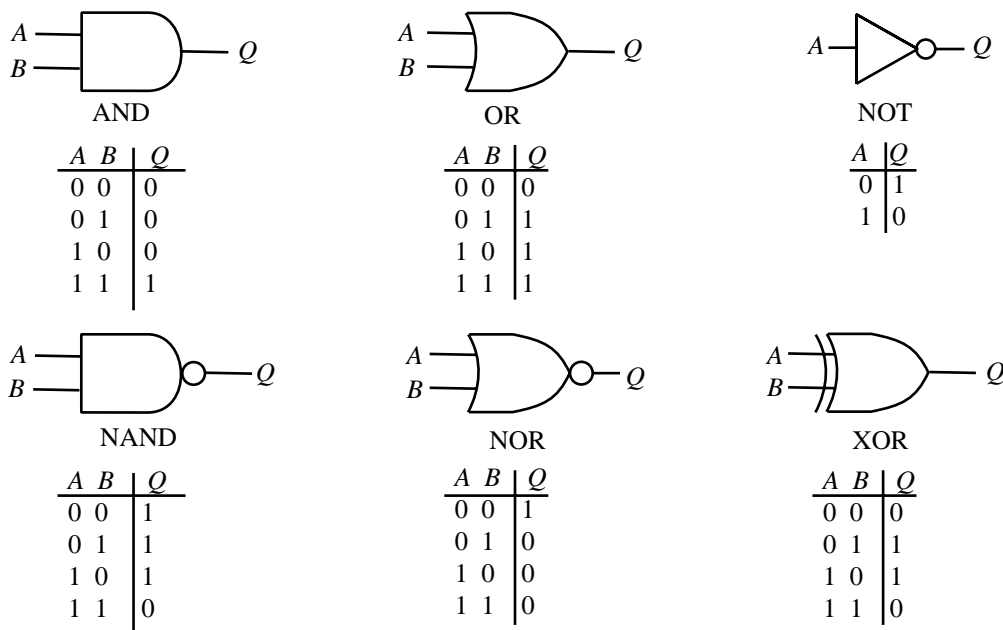


Fig. 1 Standard logic symbols and truth tables.

 


Fig. 2 Logic to generate a stopping-particle signal and corresponding truth table.

similar ones, have been implemented in electronic circuitry, where truth values can be represented by different voltage levels. The standard circuit symbols are also shown in Fig. 1.

By combining the basic operations we can construct other logical functions. For example, suppose we wish to determine whether or not a particle has stopped in a target, using the configuration of counters shown in Fig. 2. A particle passing through a counter makes the corresponding output true, and we assume the particle has stopped in the target if  $A$  and  $B$  are both true, but  $C$  is false. Formally, we want to know when the compound statement  $A \bullet B \bullet \bar{C}$  is true. An electronic implementation of the compound statement is also shown in Fig. 2, together with a truth table. Examination of the truth table shows that  $A \bullet B \bullet \bar{C}$  is true in exactly one situation, which corresponds to the physically desired result.

Sometimes it is not obvious how to write down the required expression and implement it. You might discover an implementation using only standard operations by trial and error, but it is possible to be more systematic. For example, suppose we wish to make an exclusive-OR function using AND, OR and NOT gates. To do this we can try to combine some statements that are true for exactly one combination of  $A$  and  $B$ . Consider the following:

$$\begin{aligned}
 A \bullet B &\text{ is true only when } A = 1 \text{ and } B = 1 \\
 A \bullet \bar{B} &\text{ is true only when } A = 1 \text{ and } B = 0 \\
 \bar{A} \bullet B &\text{ is true only when } A = 0 \text{ and } B = 1 \\
 \bar{A} \bullet \bar{B} &\text{ is true only when } A = 0 \text{ and } B = 0
 \end{aligned}
 \tag{1}$$

The middle two lines are the  $A, B$  values for which the X-OR is true, so if we combine them with an OR, we get the desired result,

$$A \oplus B = (\bar{A} \bullet B) + (A \bullet \bar{B}) \quad (2)$$

This procedure, combining AND statements which are true for the desired true outputs, is actually quite general, although it may generate very cumbersome expressions.

It is sometimes desirable to transform a logical expression to some other form, perhaps to simplify implementation or to take advantage of the devices available in a particular logic family. Fortunately, the logical operators define an algebra, usually referred to as Boolean algebra. The familiar commutative, associative and distributive properties hold:

$$A + B = B + A \quad A \bullet B = B \bullet A \quad (3)$$

$$A \bullet (B \bullet C) = (A \bullet B) \bullet C \quad A + (B + C) = (A + B) + C \quad (4)$$

$$A \bullet (B + C) = A \bullet B + A \bullet C \quad (5)$$

so one can use the normal rules of algebraic manipulation on logical expressions. Two theorems, called DeMorgan's laws are particularly useful:

$$\overline{A + B} = \bar{A} \bullet \bar{B} \quad \overline{A \bullet B} = \bar{A} + \bar{B} \quad (6)$$

As an example, suppose we wish to implement the exclusive-or expression using NAND gates, which compute  $\overline{A \bullet B}$ . We first attack the  $A \bullet \bar{B}$  term by adding zero, using the distributive law and then applying DeMorgan's law:

$$\begin{aligned} A \bullet \bar{B} &= A \bullet \bar{B} + A \bullet \bar{A} \\ &= A \bullet (\bar{A} + \bar{B}) \\ &= A \bullet (\overline{A \bullet B}) \end{aligned} \quad (7)$$

Doing the same with  $\bar{A} \bullet B$ , we arrive at

$$A \oplus B = [B \bullet (\overline{A \bullet B})] + [A \bullet (\overline{A \bullet B})] \quad (8)$$

We then double-negate and apply DeMorgan again to get

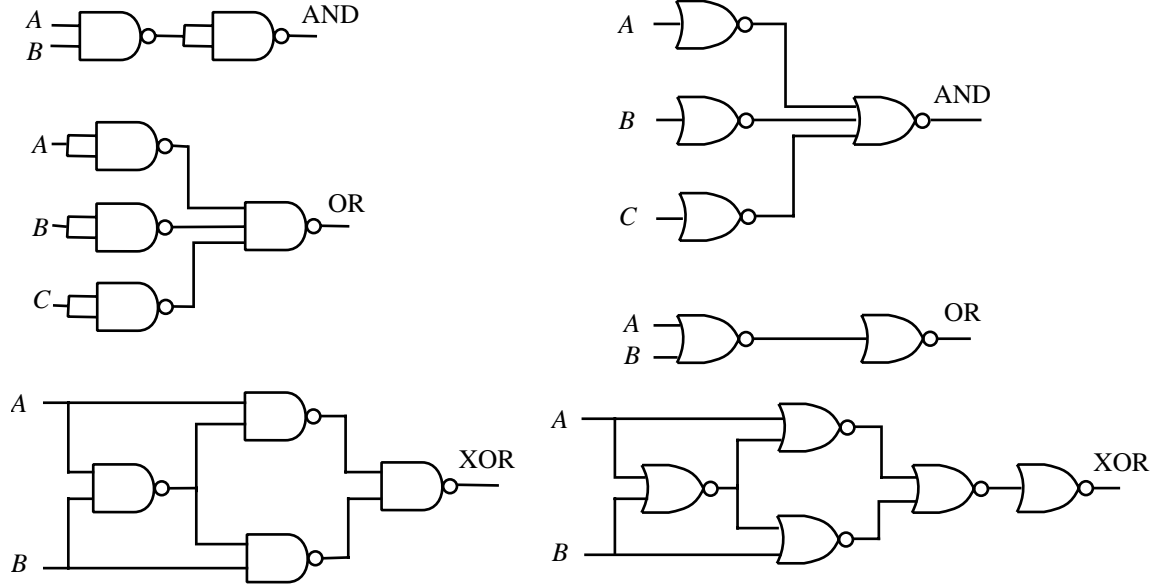


Fig 3 NAND/NOR implementation of some logic functions.

$$A \oplus B = \overline{\overline{B \cdot (A \cdot B)}} \cdot \overline{\overline{A \cdot (A \cdot B)}} \quad (9)$$

which is the desired expression in terms of NAND functions. This circuit is shown in Fig. 3, along with several other examples.

Synthesis of desired logic functions can obviously become quite complex. Fortunately there are far more sophisticated techniques available. Some of these can be found in the book by Horowitz and Hill, and others in electrical engineering texts.

## B. Time dependence

In certain systems timing may become critical. Gates require a finite amount of time to change their output in response to a change in the input signals (gate delay). In a complicated circuit it may happen that the inputs to a particular gate have been processed through different numbers of preceding stages, and may not arrive at the same time. This will cause the last gate to produce an electrically correct but logically wrong output, at least transiently. In situations where this causes problems it can be cured either by accurate matching of the signal delays, or by clocking.

The matching approach is used where the logic must handle events in "real time", as required in a particle-counting experiment. The method is to add delay as needed to insure that all possible signals require the same amount of time to propagate through each stage in the system. Timed logic circuits are sometimes called "combinational" or "asynchronous" logic,

since they produce an output as quickly as possible after a change in input. Such circuits are obviously very difficult to adjust if they are at all complex.

The alternative to asynchronous logic is "synchronous" or "clocked" logic. In this scheme an additional input, the clock, is provided at each logical stage. The circuits are designed to accept input on, say, a low to high transition of the clock signal and to change output state on the following high to low transition. This scheme always leads to valid inputs at each successive stage as long as the clock period is longer than the longest propagation delay in the system. The timing problem is then reduced to distributing the clock signal synchronously to all stages, at the cost of a slower response to the inputs.

### C. Flip-flops and counters

Flip-flops are circuits that can be put into one of two stable states with a pulse applied to a specified input. The circuit then remains in that state until another pulse is received. This constitutes a form of memory, in that the circuit "remembers" that a pulse was applied sometime in the past. An obvious application is in computer memory chips, where millions of flip-flops are put on a single integrated circuit.

The truth table for a simple example, called a set-reset (SR) flip-flop is shown in Fig. 4, together with a realization using NOR gates. The operation of the SR can be understood by reading through the truth table. If both  $S$  and  $R$  inputs are zero, the  $Q$  and  $\bar{Q}$  outputs retain whatever state they are in. If either  $S$  or  $R$  goes to 1,  $Q$  and  $\bar{Q}$  change to the values indicated and remain in that state when  $S$  or  $R$  returns to zero. If both  $S$  and  $R$  go to 1 the output is indeterminate, so that combination of inputs is not allowed.

The limitations of the SR flip-flop led to the development of several other types, of which only the JK will be examined here. The JK flip-flop can be toggled between its two states by applying pulses to a single clock input, rather than to two inputs as with the SR. More subtle differences are that the output is well-defined for all combinations of inputs, and that the output changes only at a defined time in the clock cycle. These advantages are achieved by linking two SR flip-flops in a master-slave relationship, as shown in Fig. 5. Gates 3 and 4 control the transfer of data from master to slave, while gates 7 and 8 control when the master will accept external

 


Fig. 4 SR flip-flop and a realization in NOR gates.

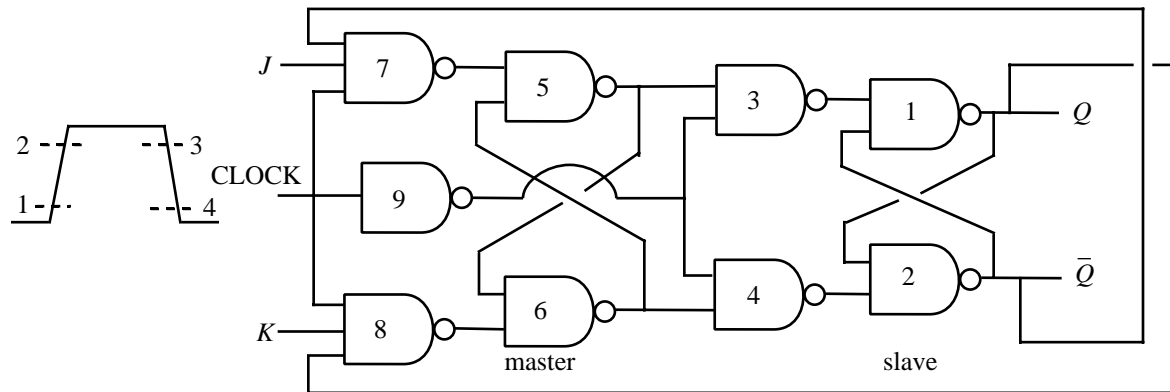


Fig. 5 JK flip-flop constructed from NAND gates. At level 1 on the clock pulse gates 3 and 4 close isolating slave from master. At level 2, 7 and 8 open connecting master to input and master may change state. At level 3 gates 7 and 8 close to isolate the master. At level 4 gates 3 and 4 open allowing the slave to change state.

inputs. The action of the gates during the clock cycle is explained in the figure. The J and K inputs function like the S and R inputs to force a particular state of the flip-flop. Finally, the output is connected back to the input so that the circuit will toggle in response to clock pulses when J and K are held at logic 1.

A binary counter can be made by connecting the output of one flip-flop to the clock input of another. A chain of  $n$  flip-flops will have  $2^n$  different output states. Each arriving clock pulse will either increment or decrement the output state by one unit, depending on the device used. A counter can be used to count the number of clock pulses arriving in a certain interval, to divide an input frequency by  $n$ , or to provide one output pulse for  $2^n$  input pulses. (These last two applications are why counters are sometimes referred to as dividers.) Standard ICs often provide additional inputs to set the counter to a specific state or to control counting.

 


Fig. 6 Timing diagram for a binary counter.

Since counters and flip-flops have inherent time dependence, truth tables do not provide sufficient information about when changes of logic state occur. They can be supplemented by a timing diagram, as given in Fig. 6 for a typical binary counter. Using the diagram, one can decipher how the outputs  $Q_A...Q_D$  respond to pulse inputs on the "clear" and "clock" lines. Note, for example, that  $Q_A$  always changes state on the falling ( $1 \rightarrow 0$ ) edge of the clock pulse.

#### D. Logic families

There are a number of commonly-available electronic logic families, as summarized in Table I. (NIM logic is a special case included for completeness. It will be considered more fully in the section on particle counting.) As you can see, the types differ in their elementary function and in whether they respond to current or voltage signals. Fan-out refers to the ability of an output to drive more than one subsequent input, but this is not usually a problem. From a design perspective, the speed of operation is often a deciding factor, along with cost and the ability to construct very complex single-chip circuits (Very Large Scale Integration).

You should also be aware that there are many ready-made functions available in each of the commercial logic families. These typically include multi-input gates, flip-flops, adder circuits

Table I. Summary of Gate Characteristics

<u>Charac.</u>	<u>Gate Type</u>				
	<u>TTL</u>	<u>ECL</u>	<u>CMOS</u>	<u>NIM(neg)</u>	<u>NIM(pos)</u>
Basic func.	NAND	OR,NOR	NOR	-	-
Connection	Current	Voltage	Voltage	Current	Voltage
Logic 0	0.0 $\rightarrow$ 0.8V	-0.9V	0 $\rightarrow$ 2V	+1 $\rightarrow$ -2mA	1.5 $\rightarrow$ -2V
1	2.5 $\rightarrow$ 5.0V	-1.8V	7 $\rightarrow$ 10V	4 $\rightarrow$ 12mA	3 $\rightarrow$ 12V
Fan-out	10	25	10-20	1	1-2
Gate delay	15ns	3ns	70ns	10ns	500ns
Advantages	Standard Cheap Noise immunity	Fast	Low power Very cheap VLSI	Modules Flexible Z=50 $\Omega$	Modules Flexible
Disadv.	Can't drive cable	Noise immunity	Slow Static -sensitive	Costly Bulky Fan-out	Costly Bulky

and even complete CPUs. There are also compatible interface circuits, such as display drivers, transmission line drivers, analog to digital converters and so on. For reasons of simplicity and reliability, you should make use of specialized units whenever possible.

It is highly unlikely that you will ever need to build a logic function out of discrete transistors, resistors etc., so for the present we will treat the circuits as black boxes. If you do a lot of digital design you should gain at least a rough idea of how the functions are carried out by the internal circuitry, since that will help you use the building blocks more effectively.

### **E. Connecting gates**

In real logic systems one wants to connect several gates together, so we need to examine what happens when we do this with the TTL circuits used in our lab exercises. When an output at logic high, +5V, is connected to the input of a similar gate a small current will flow due to the leakage currents of the input transistor in the driven gate. Since leakage currents are fairly small, a TTL gate can in fact drive several inputs into the "high" logic range. The situation is a little different for a low signal, since significant current must flow *out* of the driven input to hold it within the "low" range. The output stage of the driving gate does this by turning on its output transistor, thereby providing a relatively low-impedance path to ground. As a practical matter, though, the transistor in the driving gate can only pass so much current, and this limits the number of inputs that one circuit can drive to about 10. Similar considerations determine the number of inputs that each output can drive in the other logic families.

In general, the drive capability of a gate is called the "fanout". Within one logic family (TTL, ECL, CMOS, NIM ...) an output will always drive inputs up to the fanout, so electrical compatibility is assured simply by counting inputs. Connections can sometimes be made between families if the electrical characteristics are well understood, but it is usually necessary to use special devices to "translate" logic levels.

It is sometimes tempting to connect several outputs to one input in the hope of getting some sort of summing action, but this is unlikely to work. Consider the situation where two outputs are connected with one in a low state and the other high. The low output is trying to pull the connection low, but the high output and the input of the next gate will supply substantial current, perhaps exceeding the current sinking capability of the low output. Even if no damage occurs, the result is likely to be abnormal logic levels and unpredictable results.

### **F. Conversion circuits**

For digital logic to be useful in many applications there must be a transformation to or from continuously-variable "analog" signals. This function is the province of digital to analog, D/A, or analog to digital, A/D, converters. The actual design of such circuits demands complex



 


Fig. 7 Digital to analog converter using an R-2R ladder network. The switches are controlled by the digital input, from most to least significant bit.

tradeoffs among cost, speed and a multiplicity of possible error sources. Here we will mention some of the basic principles so that you can rationally choose a commercial module when you need it.

The goal of a D/A is to convert a multi-bit binary number to a proportional voltage or current. General purpose schemes typically involve switching voltage or current sources on or off under digital control and adding the results. One example is shown in Fig. 7, in which a cleverly-chosen resistor network provides a voltage proportional to the input number. A unity-gain amplifier buffers the resistor network from whatever load we wish to connect. The accuracy and speed of conversion will depend on resistor tolerances, the quality of the digitally-controlled switches, and the properties of the amplifier.

Analog to digital converters come in more varieties than D/As, but most designs depend on a comparator. The comparator circuit accepts a reference voltage and the unknown voltage, and produces a logical one output when the unknown exceeds the reference. The simplest A/D implementations provide a reference voltage corresponding to each digital output and use one comparator for each level. Logic circuitry determines the highest-level comparator that is at logic one and produces a corresponding binary code. These parallel or "flash" converters are fast, but become too cumbersome when high accuracy is needed. They do find use where speed is paramount, as in reading out tracking chambers in high energy physics experiments.

Successive-approximation converters use only one comparator in combination with a D/A converter. The D/A is given a digital code and the output is compared to the unknown voltage. The largest digital code that does not exceed the unknown is taken as the digital output value. The conversion obviously takes time, but by using a binary search sequence only  $n$  trials are needed for  $n$ -bit output, enabling a typical module to produce an eight to twelve bit conversion in a few microseconds.

Higher accuracy at lower speed is obtained from integrating converters, typified by single and dual-slope methods. In the single-slope method a current source charges a capacitor. The time required for the capacitor voltage to equal the unknown voltage is measured with a digital clock, whose output is therefore proportional to the unknown voltage. Single-slope integration is obviously sensitive to imperfections in the capacitor and comparator. Dual-slope integration charges the capacitor for a fixed time with a current proportional to the unknown voltage. The same capacitor is then discharged to zero by a known constant current. The discharge time, as measured by a digital clock again, is the converted value. Now the exact capacitor value is irrelevant, and the comparator only needs to detect zero voltage, which facilitates an automatic-zeroing scheme. Because of the accuracy (up to 16 bits) and relative noise immunity, dual-slope integration is used in all but the cheapest digital meters.