

	4	3	2	1																					
D	<table><tr><td colspan="2">Table of Contents</td></tr><tr><td>1</td><td>Title_Sheet</td></tr><tr><td>2</td><td>ZMOD-Syzygy and EEPROM</td></tr><tr><td>3</td><td>Level Shifters</td></tr><tr><td>4</td><td>USB-C</td></tr><tr><td>5</td><td>Power</td></tr><tr><td>6</td><td>LED and Debugging</td></tr></table>				Table of Contents		1	Title_Sheet	2	ZMOD-Syzygy and EEPROM	3	Level Shifters	4	USB-C	5	Power	6	LED and Debugging	D						
Table of Contents																									
1	Title_Sheet																								
2	ZMOD-Syzygy and EEPROM																								
3	Level Shifters																								
4	USB-C																								
5	Power																								
6	LED and Debugging																								
C					C																				
B					B																				
A	<table><tr><td colspan="2"></td><td colspan="2">University of Oxford Department of Physics, Central Electronics Group Denys Wilkinson Building Keble Road Oxford OX1 3RH United Kingdom</td></tr><tr><td colspan="4">TITLE ZMOD-USBC</td></tr><tr><td colspan="2">DRAWN BY Peter Hastings (Oxf)</td><td colspan="2">CHECKED BY University College London</td></tr><tr><td>SIZE A4</td><td>DWG NO EXT/UCL/001</td><td>DESIGN STATUS Draft - not released</td><td>REV 0.2</td></tr><tr><td>DATE 22/02/2024:08:47</td><td>SHEET 1</td><td>of 6</td><td>PROJECT QuARC</td></tr></table>						University of Oxford Department of Physics, Central Electronics Group Denys Wilkinson Building Keble Road Oxford OX1 3RH United Kingdom		TITLE ZMOD-USBC				DRAWN BY Peter Hastings (Oxf)		CHECKED BY University College London		SIZE A4	DWG NO EXT/UCL/001	DESIGN STATUS Draft - not released	REV 0.2	DATE 22/02/2024:08:47	SHEET 1	of 6	PROJECT QuARC	A
		University of Oxford Department of Physics, Central Electronics Group Denys Wilkinson Building Keble Road Oxford OX1 3RH United Kingdom																							
TITLE ZMOD-USBC																									
DRAWN BY Peter Hastings (Oxf)		CHECKED BY University College London																							
SIZE A4	DWG NO EXT/UCL/001	DESIGN STATUS Draft - not released	REV 0.2																						
DATE 22/02/2024:08:47	SHEET 1	of 6	PROJECT QuARC																						
	4	3	2	1																					

4

3

2

1

D

D

C


C

B

B

A

A

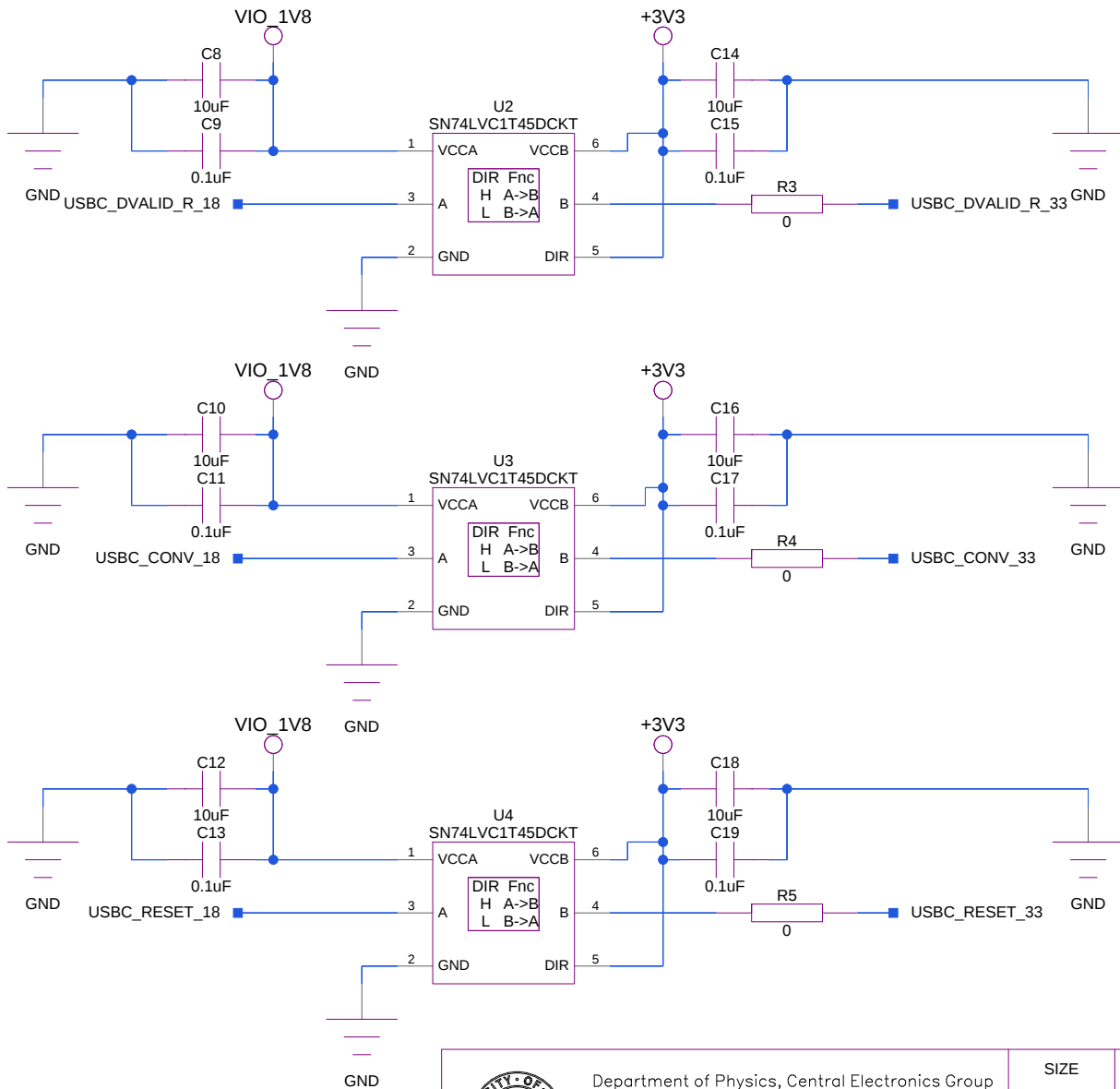

Department of Physics, Central Electronics Group
Denys Wilkinson Building
Keble Road
Oxford
OX1 3RH
United Kingdom

SIZE

A4

DRAWING NUMBER

EXT/UCL/001

Level Shifters

Title

ZMOD-USBC

REV 0.2

DATE 04/03/2024:10:40


SHEET 3 OF 6


4

3

2

1

 

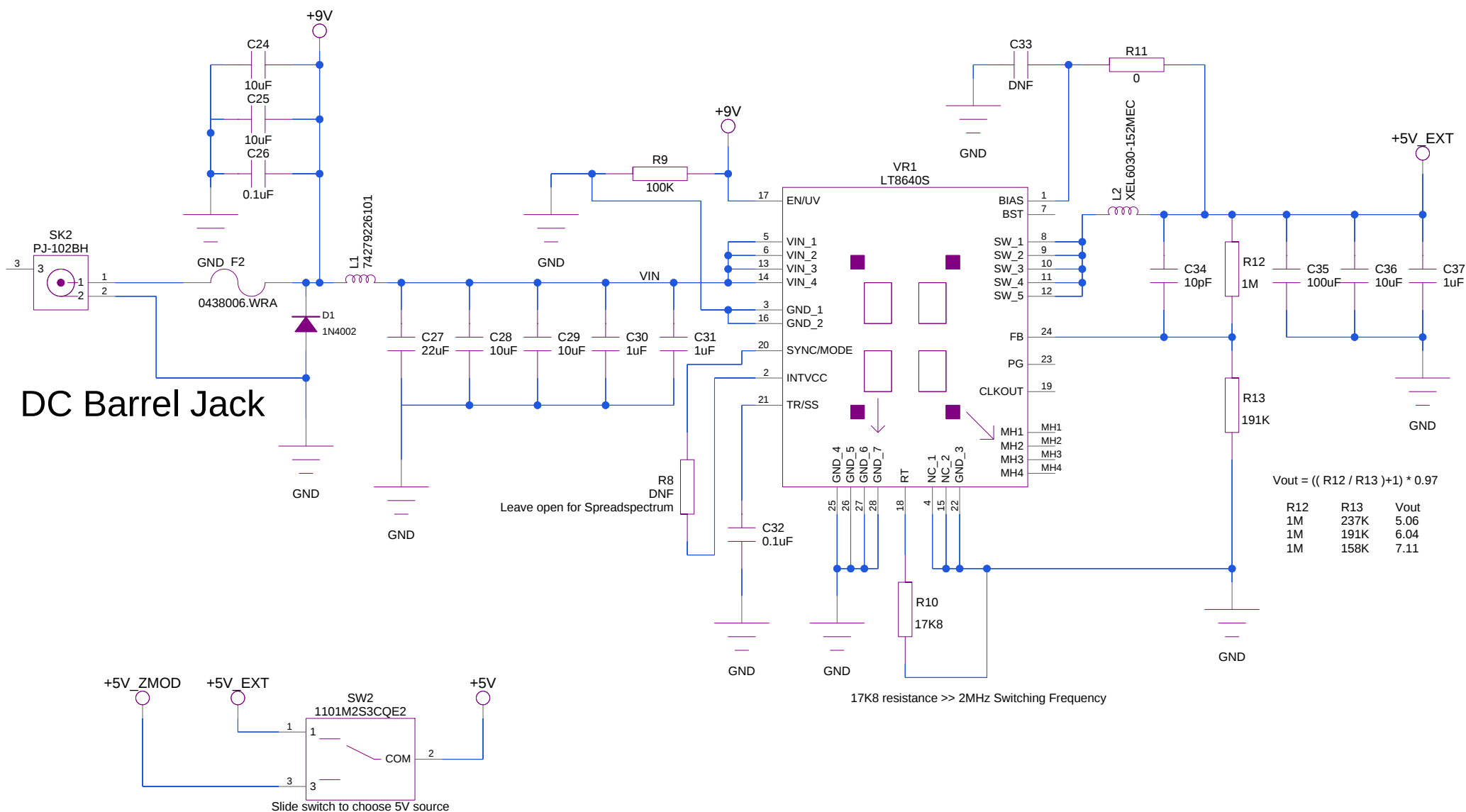

$V_{out} = ((R_{12} / R_{13}) + 1) * 0.97$

R12	R13	Vout
1M	237K	5.06
1M	191K	6.04
1M	158K	7.11

R12	R13	Vout
1M	237K	5.06
1M	191K	6.04
1M	158K	7.11

17K8 resistance >> 2MHz Switching Frequency



Department of Physics, Central Electronics Group
Denys Wilkinson Building
Keble Road
Oxford
OX1 3RH
United Kingdom

SIZE

DRAWING NUMBER

A4

EXT/UCL/001

Power

Title

ZMOD-USBC

REV 0.2

DATE 21/03/2024:07:32

SHEET 5 OF 6

4

3

2

1

D

C

B



A

D

C

B

A

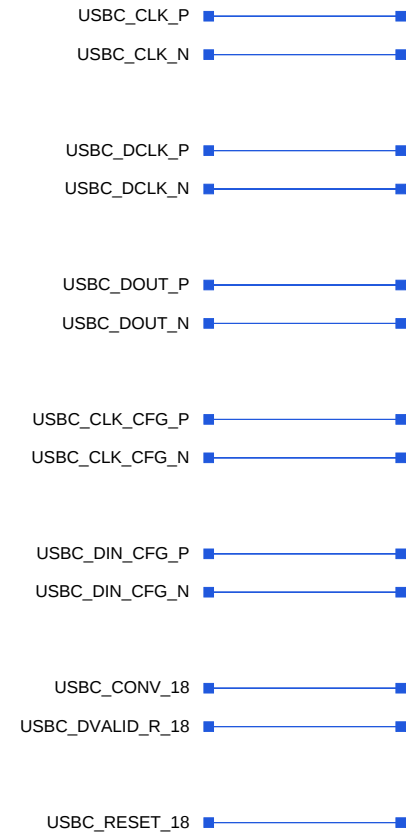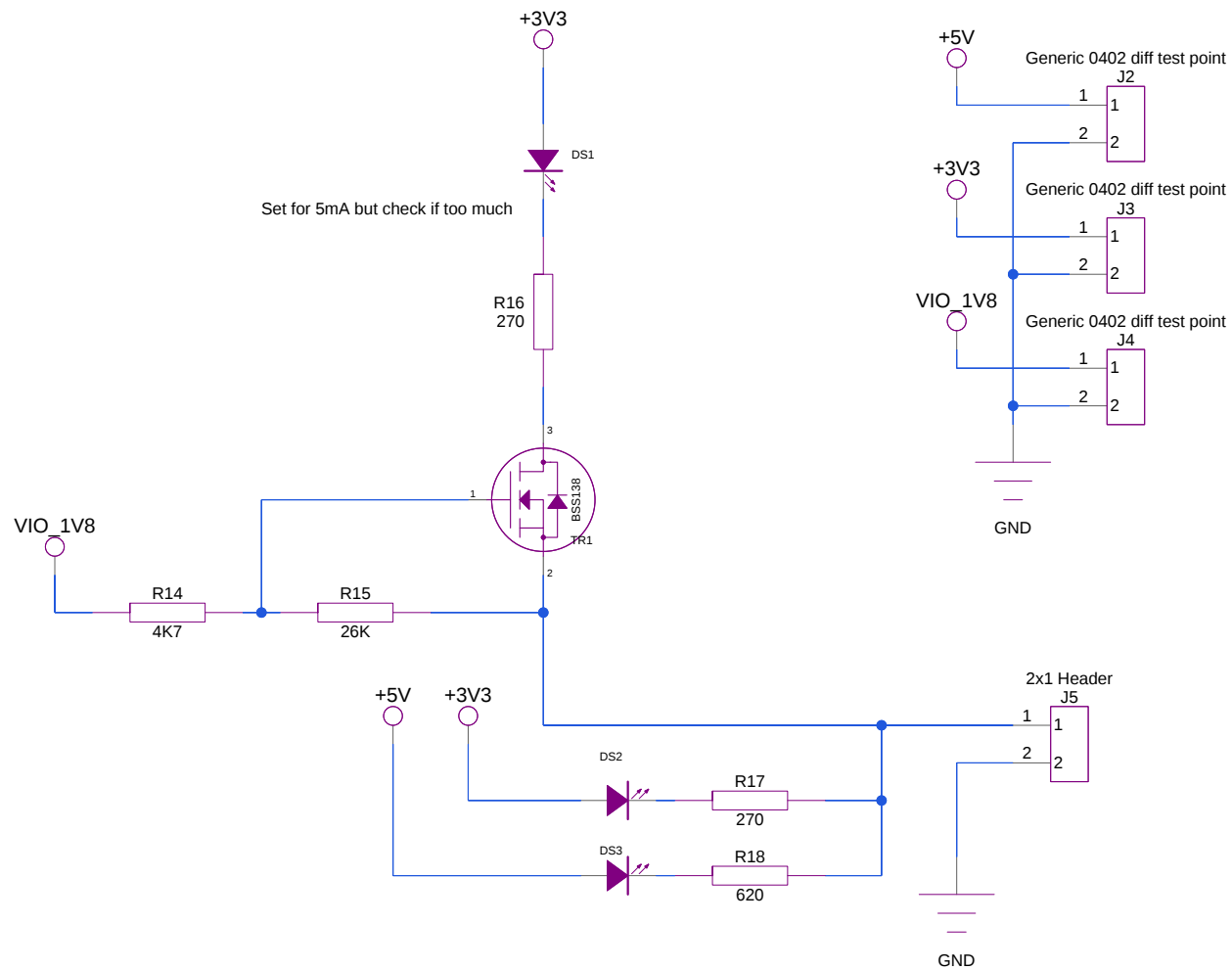

Department of Physics, Central Electronics Group
Denys Wilkinson Building
Keble Road
Oxford
OX1 3RH
United Kingdom

SIZE

A4

DRAWING NUMBER

EXT/UCL/001

LED_Debug

Title

ZMOD-USBC

REV

0.2

DATE

20/03/2024:12:18

SHEET

6

OF

6